

SPECIALITY: **COMPUTER ENGINEERING**

OPTION: **DATABASE MANAGEMENT**

EXAM PAPER: **DIGITAL ELECTRONICS**

CODE: **DBM 19**

CREDIT VALUE: 7

DURATION: **3 HOURS**

NATURE OF EXAM: WRITTEN

Answer all questions. Orderly presentation of your work is necessary. No programmable or pictured instrument is allowed.

SECTION A: NUMBER SYSTEMS AND CODES

20 mark

1) The hexadecimal number for $(95.5)_{10}$ is

- (A) $()_{16}$ 5F.8 (B) $()_{16}$ 9A.B
(C) $()_{16}$ 2E.F (D) $()_{16}$ 5A.4

2) After counting 0,1,10,11 the next binary is

- a) 12 b) 100 c) 101 d) 110

3) The number 1000_2 is equivalent to decimal number

- a) One thousand b) eight c) Four d) sixteen

4) The binary addition $1+1+1$ gives

- a) 111 b) 10 c) 110 d) 11

5) The results of binary subtraction $(100-011)$ is

- a) -111 b) 111 c) 011 d) 001

6) The $2'_s$ complement of 1000_2 is

- a) 0111 b) 0101 c) 1000 d) 0001

7) How many flip flops are required to construct a decade counter

- (A) 10 (B) 3
(C) 4 (D) 2

8) Octal coding involves grouping the bits in

- (a) 5's (b) 7's
(c) 4's (d) 3'

(a) four larger (b) three smaller
(c) three larger (d) much larger.

(a) decimal (b) binary
(c) Octal (d) hexadecimal

(a) 2 (b) 8
(c) 10 (d) 16

(a) 12 (b) 20
(c) 10 (d) 4

(a) 1101 (b) 0110
(c) 1001 (d) 1110

(A) 10001000 (C) 10000000
(B) 00001000 (D) 11000000

a) Binary b) decimal c) Octal d) hexadecimal

(A) 101110000 (B) 110110000
(C) 111010000 (D) 111100000

(A) 6793 (B) 6739
(C) 6973 (D) 6379

18) The hexadecimal number 'A0' has the decimal value equivalent to

(A) 80

(B) 256

(C) 100

(D) 160

19) The Gray code for decimal number 6 is equivalent to

(A) 1100

(B) 1001

(C) 0101

(D) 0110

20) The binary system uses powers of.....for position values

a) 2

b) 10

c) 8

d) 16

SECTION B: COMBINATIONAL LOGIC

SECTION B: COMBINATIONAL LOGIC

EXERCISE I

Simplify the Boolean function below using the Boolean algebra method

$$F(x,y,z) = \bar{x}yz + \bar{x}y\bar{z} + xz$$

1. FULL ADDER

- Draw the block diagram of a full adder
- Draw the truth table considering A, B and C_{in} as the inputs
- Bring out the output logic equations from the truth table
- Draw the logic circuit

2. MULTIPLEXER

Use an 8 – to – 1-line multiplexer to implement the Boolean expression

$$f(A, B, C) = \bar{A}.B.\bar{C} + A.\bar{B}.\bar{C} + A.B.C$$

SECTION C: SEQUENTIAL LOGIC

SECTION C : SEDUENTIAL LOGIC

EXERCISE 1

- Draw the waveform of the output Q of clocked R S flip-flop, if R and S

inputs applied to it, are as represented. The latch is initially reset

EXERCISE 2

2. Modify an asynchronous R S flip-flop so that when both the inputs R and S are 1, the flip-flop is set.